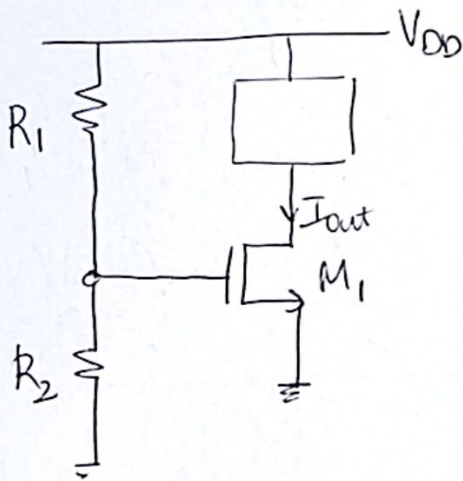


Lec 20 Current Mirrors / Biasing

Biasing

> We want to bias transistors such that the bias point is independent of Process, Voltage, Temp, (PVT).

Simplest implementation (without voltage sources).




$$I_{out} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left(\frac{R_2}{R_1 + R_2} V_{DD} - V_T \right)^2$$

↑ Temp.
 ↑ Supply
 ↑ Temp, Process


> Even if V_G is precise, I_{out} can vary!
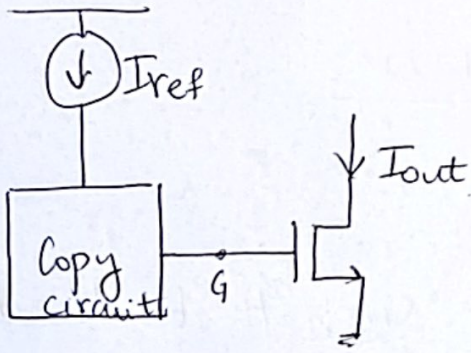
> I_{REF} "exists" → How do we copy this, i.e. how to make $I_{out} = k I_{REF}$?



Ignoring CLM
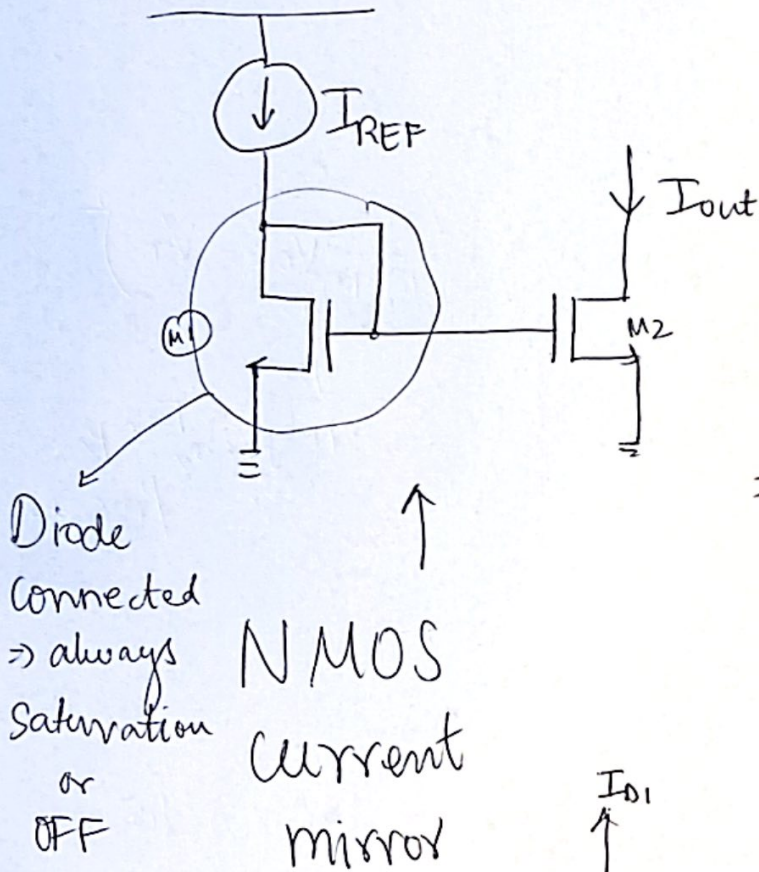
$$I_{out} = f(V_{GS}) \Rightarrow V_{GS} = f^{-1}(I_{out})$$




$$I_{REF} = \frac{1}{2} \mu_m C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_T)^2$$


$$I_{out} = \frac{1}{2} \mu_m C_{ox} \left(\frac{W}{L}\right)_2 (V_{GS} - V_T)^2$$

$$\Rightarrow I_{out} = \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} I_{REF}$$


Independent of PVT.

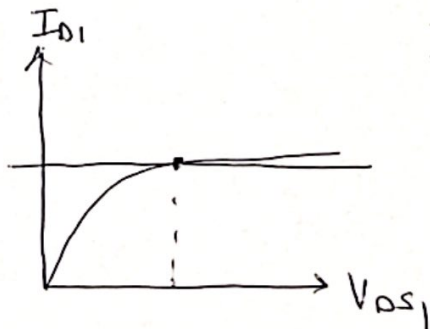

PMOS current mirrors

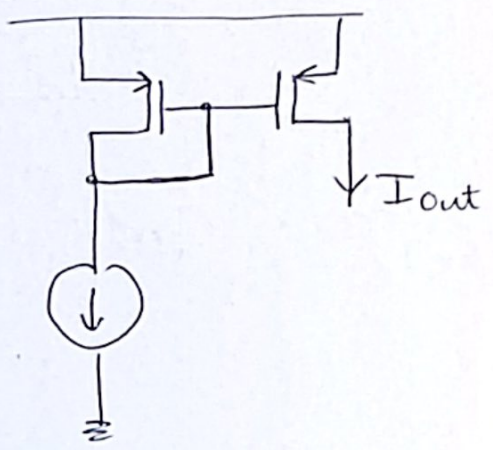


Combining

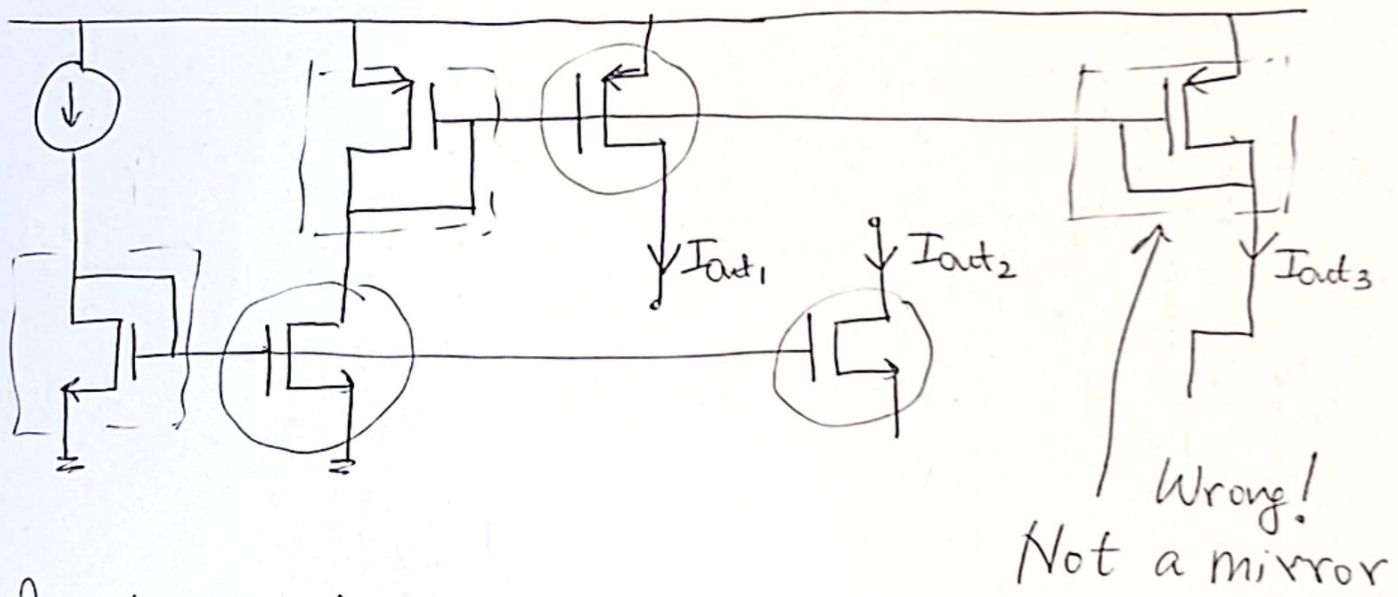


Implementation

> Mirror transistors are sized equally & copied, to prevent mismatches due to effective dimensions.
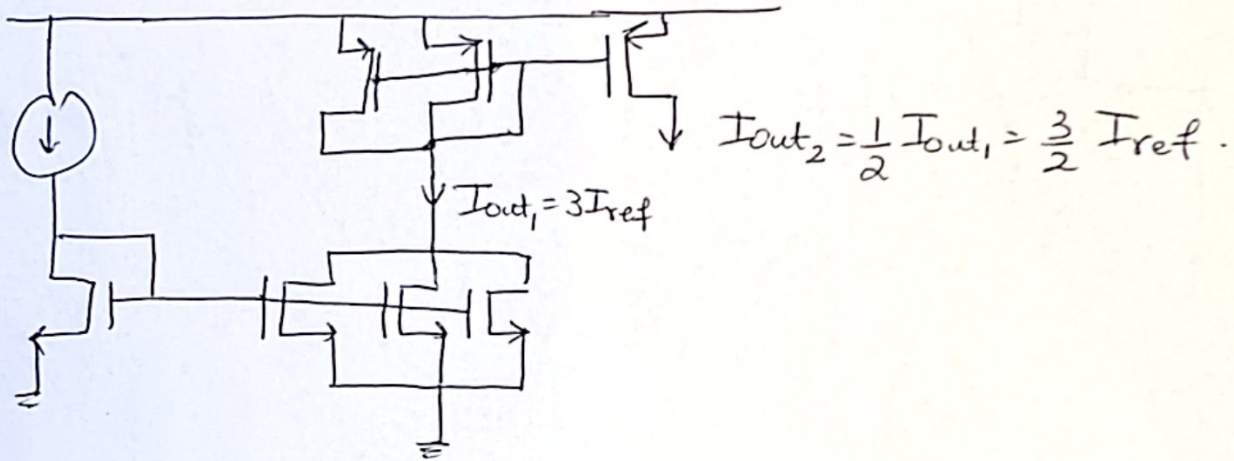
> To get noninteger current copying, use 2 levels
with $\frac{q}{p}$.



Including channel length modulation

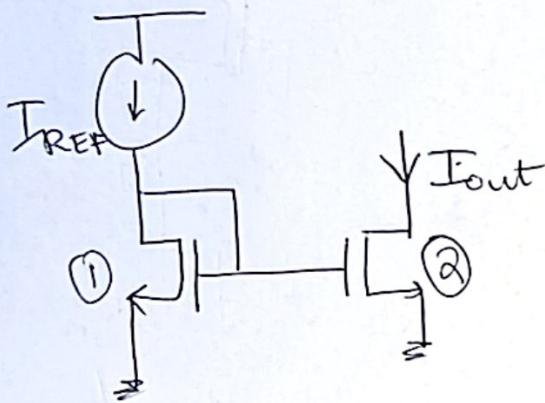

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS1})$$


$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS2})$$

$$\Rightarrow \frac{I_{D2}}{I_{D1}} = \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} \cdot \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}} \quad \leftarrow V_{GS}$$

We want $V_{DS1} = V_{DS2}$

● Try making $V_{DS1} = V_{DS2}$

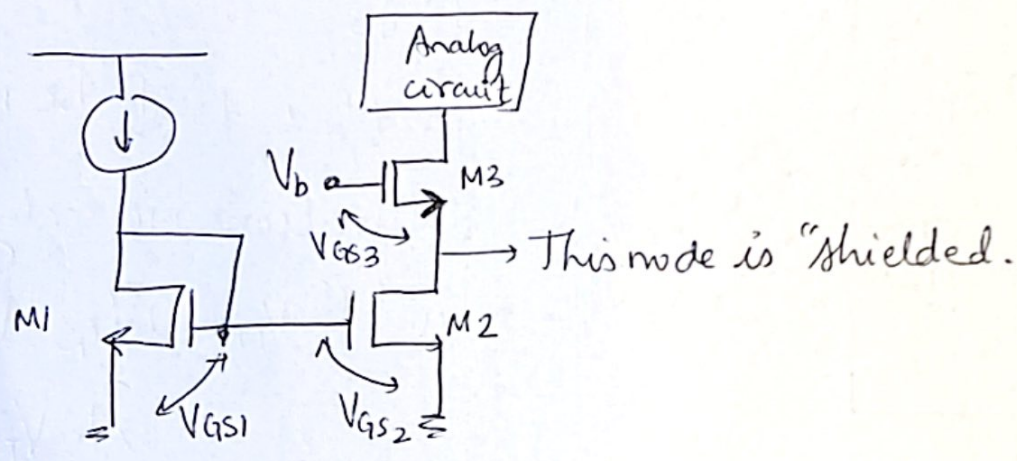
> We want ~~V_{DS2}~~ $V_{DS2} \leftarrow V_{DS1}$ & also remain independent of any external influence.



We want $V_{DS1} = V_{DS2}$

$$\underbrace{V_{DS2}}_{V_b - V_{GS3}} = \underbrace{V_{DS1}}_{V_{GS1}}$$

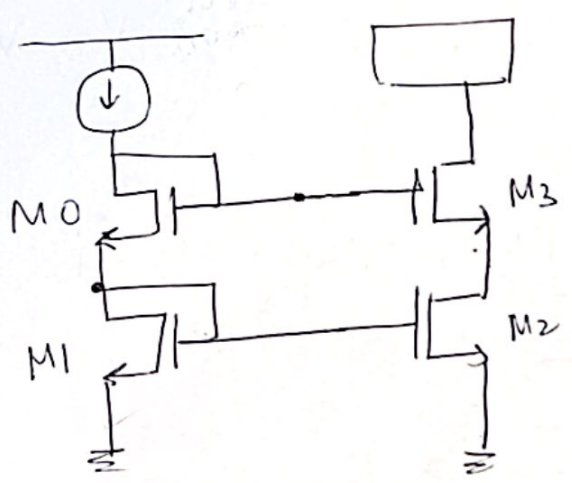$\Rightarrow V_b = V_{GS1} + V_{GS3}$ but I don't want to bias with voltage source. How do I generate $2 \times V_{GS}$?




Cascode Current Mirror

~~$V_{GS0} = V_{GS3}$~~ \Rightarrow we have $V_{DS2} = V_{DS1}$.


$\rightarrow \frac{W_3}{W_0} = \frac{W_2}{W_1}$ for nonequal mirroring.


> This consumes too much headroom!

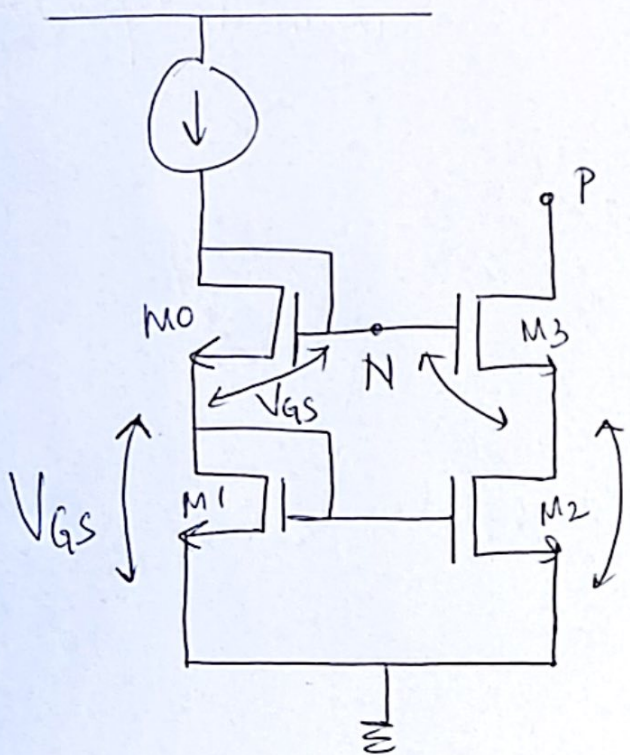

$V_N = 2V_{GS}$
 But for M_2 & M_3 to be in saturation we only need $V_N = 2V_{GS} - V_T$.
 ⇒ There is an extra V_T

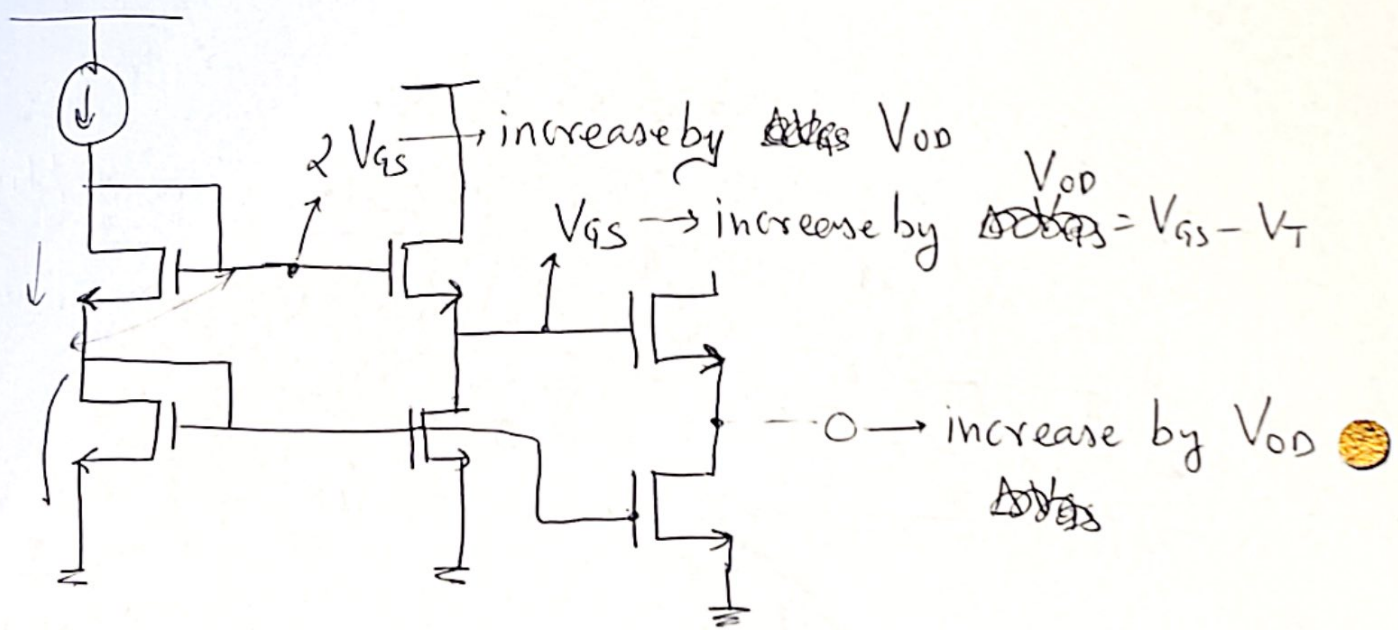$V_P = 2V_{GS} - V_T$ but it only needs to $2V_{GS} - 2V_T$.
 How can we drop another V_T ?



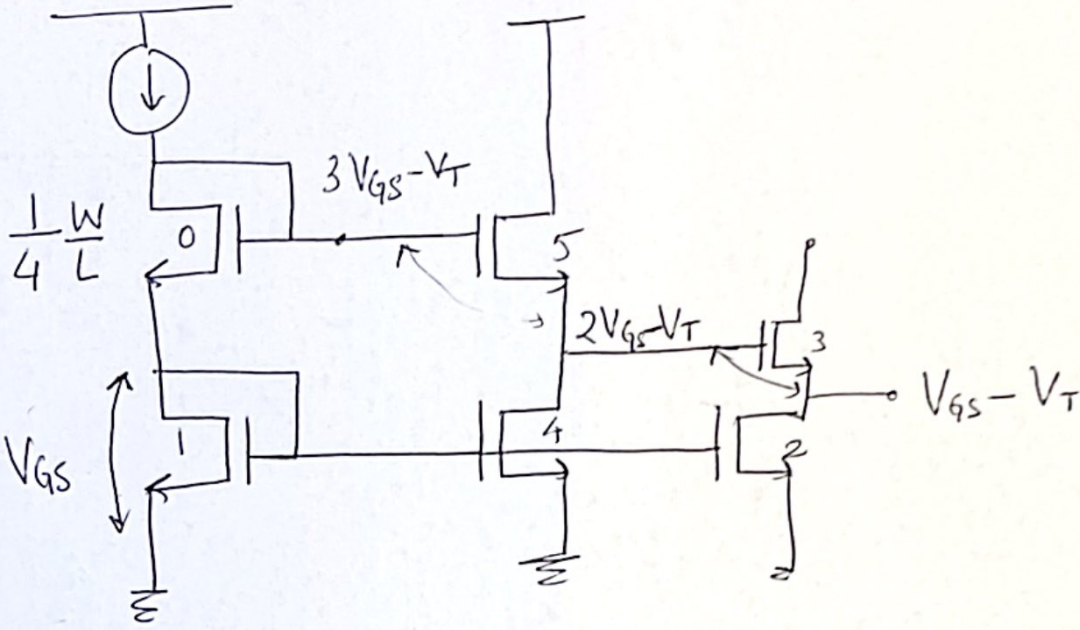

$V_{DD} = V_{GS} - V_T = \sqrt{\frac{I_D}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}}} \Rightarrow \text{if } \frac{W}{L} \text{ is } \frac{1}{4} \Rightarrow V_{DD} = 2x$

$V_{GS0} = V_T + 2 [V_{GS} - V_T]$

$= 2V_{GS} - V_T \Rightarrow V_{DS2} = V_{GS} - V_T !$